
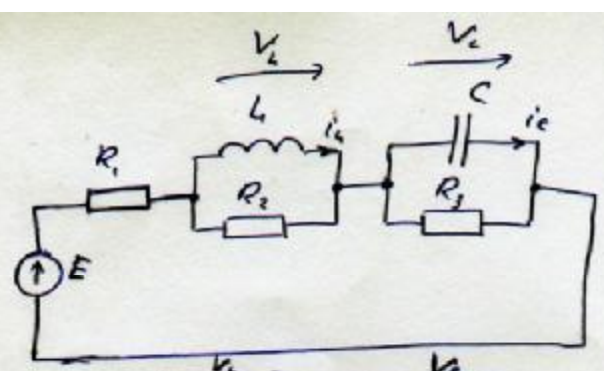


(I)

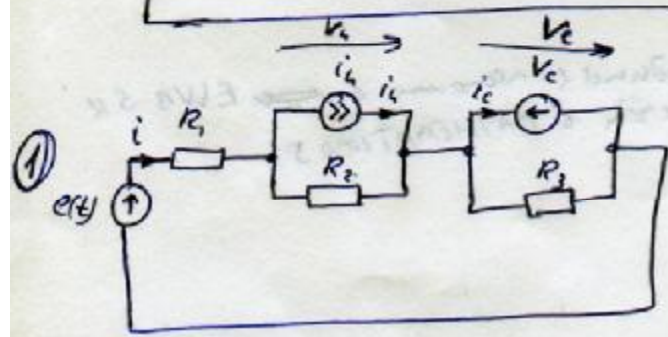

$R_1 = 34,7917 \Omega$
 $R_2 = 2,001 \cdot 10^4 \Omega$
 $R_3 = 2,004 \cdot 10^4 \Omega$
 $L = 2,829 \cdot 10^{-3} \text{ Гн}$
 $C = 4,0575 \cdot 10^{-9} \text{ Ф}$

параллельная схема и её параметры




Найти: V_L и i_C

$V_L = E - iR_1 - V_C$ i - неизвестно.
 $i_C = i - \frac{V_C}{R_3}$; i - неизвестно.


найти один из них i

1) находим i :

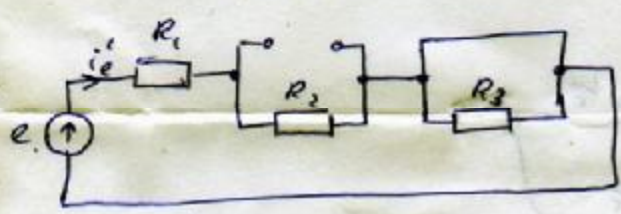


$i' = \frac{E}{R_1 + R_2}$

2) находим i_L :

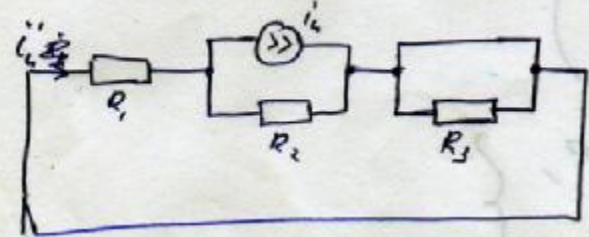


$i_L' = i_L \cdot \frac{R_2}{R_1 + R_2}$

3) находим V_C :

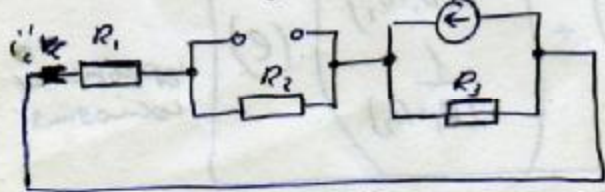

$i_C' = -\frac{V_C}{R_1 + R_2}$

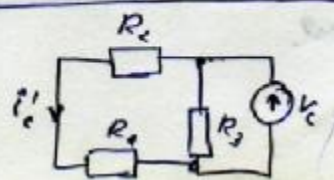$i_{C\Sigma} = i_C' + i_L' + i_C = \frac{E}{R_1 + R_2} + i_L \frac{R_2}{R_1 + R_2} - \frac{V_C}{R_1 + R_2}$



(1)

$$i = \frac{e}{R_1 + R_2} + i_L \frac{R_2}{R_1 + R_2} - \frac{V_C}{R_1 + R_2} = \frac{e + i_L R_2 - V_C}{R_1 + R_2}$$

$$\left. \begin{aligned} V_L &= e - i R_1 - V_C \\ i_C &= i - \frac{V_C}{R_3} \end{aligned} \right\}$$

$$\left. \begin{aligned} V_L &= e - R_1 \frac{e + i_L R_2 - V_C}{R_1 + R_2} - V_C \\ i_C &= \frac{e + i_L R_2 - V_C}{R_1 + R_2} - \frac{V_C}{R_3} \end{aligned} \right\}$$

(модуль и название б. ELVB 5.12
пакетом 6 MATHEMATIKA 5

③ Напишем V_L и i_C рекуррентные ПС:

$$L \frac{di_L}{dt} = e - V_C - R_1 \frac{e + i_L R_2 - V_C}{R_1 + R_2}$$

$$C \frac{dV_C}{dt} = \frac{e + i_L R_2 - V_C}{R_1 + R_2} - \frac{V_C}{R_3}$$

$$\left. \begin{aligned} L \frac{di_L}{dt} &= e - V_C - \frac{R_1}{R_1 + R_2} e - \frac{R_1 R_2}{R_1 + R_2} i_L + \frac{R_1}{R_1 + R_2} V_C \\ C \frac{dV_C}{dt} &= \frac{1}{R_1 + R_2} e + \frac{R_2}{R_1 + R_2} i_L - \frac{1}{R_1 + R_2} V_C - \frac{1}{R_3} V_C \end{aligned} \right\}$$

$$\left. \begin{aligned} L \frac{di_L}{dt} &= -\frac{R_1 R_2}{R_1 + R_2} i_L - V_C \left(1 - \frac{R_1}{R_1 + R_2}\right) + e \left(1 - \frac{R_1}{R_1 + R_2}\right) \\ C \frac{dV_C}{dt} &= \frac{R_2}{R_1 + R_2} i_L - V_C \left(\frac{1}{R_1 + R_2} + \frac{1}{R_3}\right) + \frac{1}{R_1 + R_2} e \end{aligned} \right\}$$

$$\left. \begin{aligned} \frac{di_L}{dt} &= -\frac{R_1 R_2}{L(R_1 + R_2)} i_L - \frac{R_2}{L(R_1 + R_2)} V_C + \frac{R_2}{L(R_1 + R_2)} e \\ \frac{dV_C}{dt} &= \frac{R_2}{C(R_1 + R_2)} i_L - \frac{R_1 + R_2 + R_3}{C R_3 (R_1 + R_2)} V_C + \frac{1}{C(R_1 + R_2)} e \end{aligned} \right\}$$

$$\frac{d}{dt} \begin{pmatrix} i_L \\ V_C \end{pmatrix} = \begin{pmatrix} -\frac{R_1 R_2}{L(R_1 + R_2)} & -\frac{R_2}{L(R_1 + R_2)} \\ \frac{R_2}{C(R_1 + R_2)} & -\frac{R_1 + R_2 + R_3}{C R_3 (R_1 + R_2)} \end{pmatrix} \begin{pmatrix} i_L \\ V_C \end{pmatrix} + \begin{pmatrix} \frac{R_2}{L(R_1 + R_2)} \\ \frac{1}{C(R_1 + R_2)} \end{pmatrix} (e)$$

уравнение
состояния

$$\frac{d}{dt} X = AX + BU - \text{уравнение б.д. др. состояния}$$

Pemecutan Ciri-ciri RLC.

$$\frac{di_L}{dt} = -\frac{R_1 R_2}{L(R_1 + R_2)} i_L - \frac{R_2}{L(R_1 + R_2)} V_C + \frac{R_2}{L(R_1 + R_2)} e$$

$$\frac{dV_C}{dt} = \frac{R_2}{C(R_1 + R_2)} i_L - \frac{R_1 + R_2 + R_3}{C R_3 (R_1 + R_2)} V_C + \frac{1}{C(R_1 + R_2)} e$$

$$\frac{d}{dt} X = AX + BU$$

$$X = X_0 + X_1$$

Carikan nilai pemecutan X_0 .

$$\frac{d}{dt} X = AX \quad \det(A - pE) = 0$$

$$\begin{vmatrix} -\frac{R_1 R_2}{L(R_1 + R_2)} - p & -\frac{R_2}{L(R_1 + R_2)} \\ \frac{R_2}{C(R_1 + R_2)} & -\frac{R_1 + R_2 + R_3}{C R_3 (R_1 + R_2)} - p \end{vmatrix} = 0$$

$$\left(-\frac{R_1 R_2}{L(R_1 + R_2)} - p \right) \left(-\frac{R_1 + R_2 + R_3}{C R_3 (R_1 + R_2)} - p \right) - \left(\frac{R_2}{C(R_1 + R_2)} \cdot -\frac{R_2}{L(R_1 + R_2)} \right) = 0$$

$$\left(\frac{R_1 R_2}{L(R_1 + R_2)} + p \right) \left(\frac{R_1 + R_2 + R_3}{C R_3 (R_1 + R_2)} + p \right) + \frac{R_2^2}{L C (R_1 + R_2)^2} = 0$$

$$\frac{R_1 R_2 (R_1 + R_2 + R_3)}{L C R_3 (R_1 + R_2)^2} + \frac{R_1 R_2}{L(R_1 + R_2)} p + \frac{R_1 + R_2 + R_3}{C R_3 (R_1 + R_2)} p + p^2 + \frac{R_2^2}{L C (R_1 + R_2)^2} = 0$$

$$p^2 + p \left(\frac{R_1 R_2}{L(R_1 + R_2)} + \frac{R_1 + R_2 + R_3}{C R_3 (R_1 + R_2)} \right) + \frac{R_2^2}{L C (R_1 + R_2)^2} + \frac{R_1 R_2 (R_1 + R_2 + R_3)}{L C R_3 (R_1 + R_2)^2} = 0$$

$$p^2 + p \left(\frac{R_1 R_2 R_3 C + L(R_1 + R_2 + R_3)}{L C R_3 (R_1 + R_2)} \right) + \frac{R_2^2 R_3 + R_1 R_2 (R_1 + R_2 + R_3)}{L C R_3 (R_1 + R_2)^2} = 0$$

$$2\alpha = \frac{R_1 R_2 R_3 C + L(R_1 + R_2 + R_3)}{L C R_3 (R_1 + R_2)} = 3.6052$$

$$\omega_0^2 = \frac{R_2^2 R_3 + R_1 R_2 (R_1 + R_2 + R_3)}{L C R_3 (R_1 + R_2)^2} = 8.0924 \cdot 10^7$$

(4)

(3)

$$\left(\frac{R_1 R_2}{4(R_1 + R_2)} + p \right) \left(\frac{R_1 + R_2 + R_3}{4R_3(R_1 + R_2)} + p \right) + \frac{R_2}{4(R_1 + R_2)} \cdot \frac{R_2}{4(R_1 + R_2)} = 0$$

$$p^2 + p \left(\frac{R_1 R_2}{4(R_1 + R_2)} + \frac{R_1 + R_2 + R_3}{4R_3(R_1 + R_2)} \right) + \frac{R_1 R_2 \cdot (R_1 + R_2 + R_3)}{4R_3(R_1 + R_2)^2} + \frac{R_2^2}{4(R_1 + R_2)^2} = 0$$

$$2\alpha = \frac{R_1 R_2}{4(R_1 + R_2)} + \frac{R_1 + R_2 + R_3}{4R_3(R_1 + R_2)} = \frac{4R_1 R_2 R_3 + (R_1 + R_2 + R_3)}{4R_3(R_1 + R_2)} = 3,68521$$

$$\alpha = 1,84261 = 1,84261 \cdot 10^4$$

$$\omega_0^2 = \frac{R_1 R_2 \cdot (R_1 + R_2 + R_3)}{4R_3(R_1 + R_2)^2} + \frac{R_2^2}{4(R_1 + R_2)^2} = \frac{R_1 R_2 (R_1 + R_2 + R_3) + R_2^2 \cdot R_3}{4R_3(R_1 + R_2)^2} = 8,71181 \cdot 10^{10} \text{ (rad}^2\text{/s}^2\text{)}$$

$$\omega_0 = 2,95158 \cdot 10^5 \text{ rad/s}$$

$$Q = \frac{\omega_0}{2\alpha} = \frac{2,95158 \cdot 10^5}{3,68521 \cdot 10^4} = 8,009259 \quad \text{колебания затухают слабо}$$

$$p_{1,2} = -1,84261 \cdot 10^4 \pm j \sqrt{3,3952 \cdot 10^8 - 2,95158 \cdot 10^5} = -1,84261 \cdot 10^4 \pm j 1,84261 \cdot 10^4$$

$\alpha < \omega_0$ корни p_1 и p_2 комплексно сопряженные

$$p_{1,2} = -1,84261 \cdot 10^4 \pm j \sqrt{8,71181 \cdot 10^{10} - 3,3952 \cdot 10^8} = -1,84261 \cdot 10^4 \pm j 2,9458 \cdot 10^5$$

$$p_1 = -1,84261 \cdot 10^4 + j 2,9458 \cdot 10^5$$

$$p_{1,2} = -\alpha \pm j\beta$$

$$p_2 = -1,84261 \cdot 10^4 - j 2,9458 \cdot 10^5$$

$$Q \approx \frac{\beta}{2\alpha} = \frac{2,9458 \cdot 10^5}{3,68521 \cdot 10^4} = 7,9936 \quad \text{колебания}$$

$$X_0 = \begin{pmatrix} i_L \\ v_C \end{pmatrix} = \begin{pmatrix} a_1 \\ a_2 \end{pmatrix} \cdot e^{p_1 t} + \begin{pmatrix} b_1 \\ b_2 \end{pmatrix} \cdot e^{p_2 t} \quad \vec{a} = \vec{b}$$

$$X_0 = \begin{pmatrix} i_L \\ v_C \end{pmatrix} = \begin{pmatrix} \kappa_1 \\ \kappa_2 \end{pmatrix} \cdot e^{(-\alpha + j\beta)t} + \begin{pmatrix} \kappa_1^* \\ \kappa_2^* \end{pmatrix} \cdot e^{(-\alpha - j\beta)t} \quad \left. \vphantom{\begin{pmatrix} \kappa_1 \\ \kappa_2 \end{pmatrix}} \right\} \text{комплексно сопряженные}$$

$$i_L(t) = A_I \cdot e^{-\alpha t} \cdot \cos(\beta t + \varphi_I)$$

$$v_C(t) = A_V \cdot e^{-\alpha t} \cdot \cos(\beta t + \varphi_V)$$

$$R_1 = 34,797$$

$$R_3 = R_2 = 2,004 \cdot 10^4$$

$$R_3 L = 2,829 \cdot 10^{-3}$$

$$C = 4,0575 \cdot 10^{-9}$$

$$\frac{1}{LC} - \frac{R_3}{R_3 LC} = \frac{R_3 - R_1}{LC R_3} = 2,6967 \cdot 10^{10} \text{ rad/s} \quad \textcircled{\text{III}}$$

$$\frac{1}{R_1 C} + \frac{1}{R_3 C} + \frac{R_1}{R_2 R_3 C} - \frac{R_1}{L} = \textcircled{\text{I}}$$

$$\left. \begin{aligned} V_1: \quad \frac{V_1 - e}{R_1} + \frac{V_1 - V_2}{R_2} + \frac{1}{L} \int_{-\infty}^t (V_1 - V_2) dt &= 0 \\ V_2: \quad \frac{V_2 - V_1}{R_2} + \frac{1}{L} \int_{-\infty}^t (V_2 - V_1) dt + \frac{V_2}{R_3} + C \frac{dV_2}{dt} &= 0 \end{aligned} \right\}$$

$$\left. \begin{aligned} \frac{1}{R_1} \frac{dV_1}{dt} - \frac{1}{R_1} \frac{de}{dt} + \frac{1}{R_2} \frac{dV_1}{dt} - \frac{1}{R_2} \frac{dV_2}{dt} + \frac{1}{L} (V_1 - V_2) &= 0 \\ \frac{1}{R_2} \frac{dV_2}{dt} - \frac{1}{R_2} \frac{dV_1}{dt} + \frac{1}{L} (V_2 - V_1) + \frac{dV_2}{dt R_3} + C \frac{d^2 V_2}{dt^2} &= 0 \end{aligned} \right\}$$

$$\left. \begin{aligned} \text{I} \quad \frac{pV_1}{R_1} - \frac{pe}{R_1} + \frac{pV_1}{R_2} - \frac{pV_2}{R_2} + \frac{V_1}{L} - \frac{V_2}{L} &= 0 \\ \text{II} \quad \frac{pV_2}{R_2} - \frac{pV_1}{R_2} + \frac{V_2}{L} - \frac{V_1}{L} + \frac{pV_2}{R_3} + C p^2 V_2 &= 0 \end{aligned} \right\}$$

$$V_L = V_1 - V_2 \quad \textcircled{\text{II}} \Rightarrow V_1 = V_L + V_2$$

einsetzen:

$$\left. \begin{aligned} \frac{pV_L}{R_1} + \frac{pV_2}{R_1} - \frac{pe}{R_1} + \frac{pV_L}{R_2} + \frac{pV_2}{R_2} - \frac{pV_2}{R_2} + \frac{V_L}{L} + \frac{V_2}{L} - \frac{V_2}{L} &= 0 \\ \frac{pV_2}{R_2} - \frac{pV_L}{R_2} - \frac{pV_2}{R_2} + \frac{V_L}{L} - \frac{V_2}{L} - \frac{V_2}{L} + \frac{pV_2}{R_3} + C p^2 V_2 &= 0 \end{aligned} \right\}$$

$$\left. \begin{aligned} \text{I} \quad \frac{pV_L}{R_1} + \frac{pV_2}{R_1} - \frac{pe}{R_1} + \frac{pV_L}{R_2} + \frac{V_L}{L} &= 0 \\ \text{II} \quad \frac{pV_2}{R_2} - \frac{V_L}{L} + \frac{pV_2}{R_3} + C p^2 V_2 &= 0 \end{aligned} \right\}$$

$$\left. \begin{aligned} \frac{pV_L}{R_1} + \frac{pV_L}{R_2} + \frac{V_L}{L} + \frac{pV_2}{R_1} - \frac{pe}{R_1} &= 0 \\ - \frac{pV_L}{R_2} - \frac{V_L}{L} + \frac{pV_2}{R_3} + C p^2 V_2 &= 0 \end{aligned} \right\}$$

$$\text{III} \quad \frac{pV_2}{R_1} - \frac{pe}{R_1} - V_L \left(\frac{p}{R_1} + \frac{p}{R_2} + \frac{1}{L} \right)$$

$$V_2 = e - V_L \left(1 + \frac{R_1}{R_2} + \frac{R_1}{L} \right)$$

нодмателен V_2 из I и II.

$$V_2 = e - V_L \left(1 + \frac{R_1}{R_2} + \frac{R_1}{pR_3L} \right)$$

$$\text{II} - \frac{pV_L}{R_2} - \frac{V_L}{L} + \frac{pV_2}{R_3} + p^2CV_2 = 0$$

$$-\frac{pV_L}{R_2} - \frac{V_L}{L} + \frac{e}{R_3} - V_L \left(\frac{1}{R_3} + \frac{R_1}{R_2R_3} + \frac{1}{pR_3L} \right) + p^2Ce - p^2CV_L \left(1 + \frac{R_1}{R_2} + \frac{1}{pR_3L} \right) = 0$$

$$\frac{pV_L}{R_2} + \frac{V_L}{L} + V_L \left(\frac{1}{R_3} + \frac{R_1}{R_2R_3} + \frac{1}{pR_3L} \right) + V_L \left(p^2C + \frac{p^2CR_1}{R_2} + \frac{pC}{R_3L} \right) = \frac{e}{R_3} + p^2Ce$$

$$\text{III} - \frac{pV_L}{R_2} - \frac{V_L}{L} + \frac{pe}{R_3} - \frac{pV_L}{R_3} - \frac{pV_L R_1}{R_2 R_3} - \frac{pR_1 V_L}{R_3 L} + p^2Ce - p^2CV_L - \frac{p^2CR_1}{R_2} - \frac{pCV_L R_1}{L} = 0$$

$$-\frac{pV_L}{R_2} - \frac{V_L}{L} - \frac{pV_L}{R_3} \left(1 + \frac{R_1}{R_2} + \frac{R_1}{pL} \right) - p^2CV_L \left(1 + \frac{R_1}{R_2} + \frac{R_1}{pL} \right) = \frac{pe}{R_3} - p^2Ce$$

$$\frac{pV_L}{R_2} + \frac{V_L}{L} + \frac{pV_L}{R_3} \left(1 + \frac{R_1}{R_2} + \frac{R_1}{pL} \right) + p^2CV_L \left(1 + \frac{R_1}{R_2} + \frac{R_1}{pL} \right) = \frac{pe}{R_3} + p^2Ce$$

$$\frac{pV_L}{R_2} + \frac{V_L}{L} + \frac{pV_L}{R_3} + \frac{pR_1 V_L}{R_2 R_3} + \frac{R_1 V_L}{R_3 L} + p^2CV_L + \frac{p^2CR_1 V_L}{R_2} + \frac{p^2CR_1 V_L}{L} = \frac{pe}{R_3} + p^2Ce$$

$$p \frac{V_L}{R_2 C} + \frac{V_L}{LC} + p \frac{V_L}{R_3 C} + p \frac{R_1 V_L}{R_2 R_3 C} + \frac{R_1 V_L}{R_3 LC} + p^2 V_L + \frac{p^2 R_1 V_L}{R_2} + \frac{p^2 R_1 V_L}{L} = \frac{pe}{R_3 C} + p^2 Ce$$

$$p^2 \left(V_L + \frac{R_1 V_L}{R_2} \right) + p \left(\frac{V_L}{R_2 C} + \frac{R_1 V_L}{R_2 R_3 C} + \frac{R_1 V_L}{R_3 L} \right) + \frac{V_L}{LC} + \frac{R_1 V_L}{R_3 LC} = \frac{pe}{R_3 C} + p^2 Ce$$

$$p^2 \left(1 + \frac{R_1}{R_2} \right) + p \left(\frac{1}{R_2 C} + \frac{R_1}{R_2 R_3 C} + \frac{R_1}{L} \right) + \left(\frac{1}{LC} + \frac{R_1}{R_3 LC} \right) = 0$$

$$p^2 + p \left(\frac{\frac{1}{R_2 C} + \frac{R_1}{R_2 R_3 C} + \frac{R_1}{L}}{1 + \frac{R_1}{R_2}} \right) + \left(\frac{\frac{1}{LC} + \frac{R_1}{R_3 LC}}{1 + \frac{R_1}{R_2}} \right) = 0 \quad \checkmark$$

$$2\omega = 36852,1 \text{ V}$$

$$\omega = 18426,1 = 1,84261 \cdot 10^5$$

$$\omega_0^2 = 8,7118 \cdot 10^9 \text{ V}$$

$$\omega_0 = 295158 \cdot 10^5 \text{ rad/s}$$

6

"In-Out"

(IV)

$$\frac{d^2 V_L}{dt^2} \left(1 + \frac{R_1}{R_2}\right) + \frac{dV_L}{dt} \left(\frac{1}{R_2 C} + \frac{1}{R_3 C} + \frac{R_1}{R_2 R_3 C} + \frac{R_1}{L}\right) + V_L \left(\frac{1}{LC} + \frac{R_1}{R_3 LC}\right) = \frac{d^2 e}{dt^2} + \frac{de}{dt} \frac{1}{R_3 C}$$

$$P_{1,2} = -1,34261 \cdot 10^4 \pm j 2,9450 \cdot 10^5$$


" α "

" β "

$$R_3 = R_2$$

~~Handwritten scribbles~~

Помогите

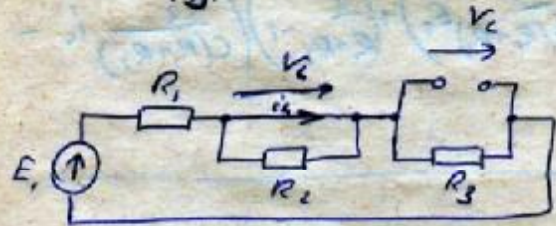

$$\begin{aligned} I_L &= i_L(0^-) = \frac{E_1}{R_1 + R_3} \\ V_L &= V_L(0^-) = E_1 \cdot \frac{R_3}{R_1 + R_3} \end{aligned} \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{установившееся значение в момент времени } 0^-$$

$$V_L(0^+) = V_L(0^-) - V_L(0^-)$$

$$i_L(0^+) = i_L(0^-) - i_L(0^-)$$

$$V_L = E - R_1 \cdot \frac{E + I_L R_2 - V_L}{R_1 + R_2} - V_L$$

$$V_L(0^+) = E_1 - R_1 \cdot \frac{E_1 + \frac{E_1 R_2}{R_1 + R_3} - \frac{E_1 R_3}{R_1 + R_3}}{R_1 + R_2} - \frac{E_1 R_3}{R_1 + R_3}$$

$$V_L(0^+) = E_1 - \frac{E_1 R_1}{R_1 + R_2} \cdot \frac{R_1 + R_2}{R_1 + R_3} + \frac{E_1 R_1 R_2}{(R_1 + R_2)(R_1 + R_3)} - \frac{E_1 R_3}{R_1 + R_3}$$

$$\begin{aligned} V_L(0^+) &= E_2 - \frac{R_1}{R_1 + R_2} \left(E_2 + \frac{E_1 R_3}{R_1 + R_3} - \frac{E_1 R_3}{R_1 + R_3} \right) - \frac{E_1 R_3}{R_1 + R_3} \\ &= E_2 - \frac{R_1}{R_1 + R_2} \left(\frac{R_1 E_2 + R_3 E_2 + E_1 R_2 - E_1 R_3}{R_1 + R_3} \right) - \frac{E_1 R_3}{R_1 + R_3} \\ &= E_2 - \frac{R_1 (E_1 R_2 - E_1 R_3 + E_2 R_1 + E_2 R_3)}{(R_1 + R_2)(R_1 + R_3)} - \frac{E_1 R_3}{R_1 + R_3} \end{aligned}$$

$$V_L(0^+) = \frac{R_1^2 E_2 + R_1 R_3 E_2 + R_2 R_3 E_2 + R_1 R_2 E_1 - R_1 R_3 E_1 - R_3^2 E_1}{(R_1 + R_2)(R_1 + R_3)} - \frac{E_1 R_3}{R_1 + R_3}$$

(7)

$$V_b = E - \frac{R_1 E}{R_1 + R_2} - \frac{R_2}{R_1 + R_2} J_L + \frac{1}{R_1 + R_2} V_c - V_c$$

$$V_b = E - \frac{R_1 E}{R_1 + R_2} - \frac{R_2}{R_1 + R_2} J_L + \left(\frac{1}{R_1 + R_2} - 1 \right) V_c$$

$$(0^+) \frac{dV_b}{dt} = \frac{dE}{dt} - \frac{R_1}{R_1 + R_2} \frac{dE}{dt} - \frac{R_2}{R_1 + R_2} \frac{dJ_L}{dt} + \left(\frac{1}{R_1 + R_2} - 1 \right) \frac{dV_c}{dt}$$

$$\frac{dV_b(0^+)}{dt} = - \frac{R_2}{R_1 + R_2} \frac{dJ_b}{dt} + \left(\frac{1}{R_1 + R_2} - 1 \right) \frac{dV_c}{dt}$$

$$\frac{dV_b(0^+)}{dt} = - \frac{R_2}{R_1 + R_2} \left(- \frac{R_1 R_2}{L(R_1 + R_2)} i_L - \frac{R_2}{L(R_1 + R_2)} V_c + \frac{R_2}{L(R_1 + R_2)} E_2 \right) + \left(\frac{1}{R_1 + R_2} - 1 \right) \left(\frac{R_2}{C(R_1 + R_2)} i_L - \frac{R_2 + R_2 + R_3}{C R_3 (R_1 + R_2)} V_c + \frac{1}{C(R_1 + R_2)} E_2 \right)$$

Substituiert in 4y

$$V_b(t) = K e^{(-\alpha + j\beta)t} + K^* e^{(-\alpha - j\beta)t} = 2 \operatorname{Re} K$$

$$V_b(t) = E_2 - \frac{R_1}{R_1 + R_2} \left(\frac{E_1 R_2 - E_1 R_3 + E_2 R_1 + E_2 R_3}{R_1 + R_3} \right) + \frac{E_1 R_3}{R_1 + R_3}$$

$$= \frac{E_2 (R_1 + R_2) (R_1 + R_3) - R_1 (E_1 R_2 - E_1 R_3 + E_2 R_1 + E_2 R_3) + (R_1 + R_2) (E_1 R_3)}{(R_1 + R_2) (R_1 + R_3)}$$

$$= \frac{R_1^2 E_2 + R_1 R_2 E_2 + R_1 R_3 E_2 + R_2 R_3 E_2 - R_1 R_2 E_1 - R_1 R_3 E_1 - R_2^2 E_2 - R_2 R_3 E_2 + R_1 R_2 E_1 + R_1 R_3 E_1}{(R_1 + R_2) (R_1 + R_3)}$$

$$= \frac{E_2 R_2 - E_1 R_2}{R_1 + R_2}$$

$$V_b(t) = \frac{E_2 R_2 - E_1 R_2}{R_1 + R_2}$$

$$V_b = 56,9012$$

Substituiert in 6. moniert Gleichung 0+ (also in 2. Gleichung)

$$\frac{dV_L}{dt} = -\frac{R_2}{R_1+R_2} \frac{di_L}{dt} + \left(\frac{1}{R_1+R_2} - 1\right) \frac{dV_C}{dt} =$$

$$= -\frac{R_2}{R_1+R_2} \left(\frac{-R_1 R_2 i_L - R_2 V_C + R_2 E_2}{L(R_1+R_2)} \right) + \left(\frac{1}{R_1+R_2} - 1\right) \left(\frac{R_2 R_3 i_L - (R_1+R_2+R_3)V_C + R_3 E_2}{CR_3(R_1+R_2)} \right) =$$

$$= \frac{R_2}{R_1+R_2} \left(\frac{\frac{R_1 R_2 E_1}{R_1+R_3} + \frac{R_2 R_3 E_1}{R_1+R_3} - R_2 E_2}{L(R_1+R_2)} \right) + \left(\frac{1}{R_1+R_2} - 1\right) \left(\frac{\frac{R_2 R_3 E_1}{R_1+R_3} - \frac{(R_1+R_2+R_3)R_3 E_1}{R_1+R_3} + R_3 E_2}{CR_3(R_1+R_2)} \right)$$

$$J_4 = \frac{E_1}{R_1+R_3}$$

$$V_C = \frac{E_1 R_3}{R_1+R_3}$$

$$\frac{dV_L}{dt} = -719831 \text{ - value found by inserting given } 0 \text{ (found by step)}$$

$$\frac{di_L}{dt} = -\frac{R_1 R_2 J_4}{L(R_1+R_2)} - \frac{R_2 V_C}{L(R_1+R_2)} + \frac{R_2 E_2}{L(R_1+R_2)}$$

$$\frac{dV_C}{dt} = \frac{R_2 J_4}{C(R_1+R_2)} - \frac{(R_1+R_2+R_3)V_C}{CR_3(R_1+R_2)} + \frac{E_2}{C(R_1+R_2)}$$

$$\frac{R_1 R_2 E_1}{C(R_1+R_2)(R_1+R_3)} - \frac{(R_1+R_2+R_3)R_2 E_1 R_3}{CR_3(R_1+R_2)(R_1+R_3)} + \frac{E_2}{C(R_1+R_2)} =$$

$$= \frac{R_2 R_3 E_1 - (R_1+R_2+R_3)E_1 R_3 + (R_1+R_3)R_3 E_2}{CR_3(R_1+R_2)(R_1+R_3)}$$

$$= \frac{R_2 E_1 - (R_1+R_2+R_3)E_1 + (R_1+R_3)E_2}{C(R_1+R_2)(R_1+R_3)}$$

$$\frac{dV_L}{dt} = -719831 = -7,19831 \cdot 10^5$$

$$V_L = 56,9012$$

$$ReK = 28,4506$$

$$ImK = -0,557805$$

$$K = 28,4506 - j0,557805$$

$$A = 28,4561 \cdot 2 = 56,9121$$

$$\phi_0 = \arg K = \arctan\left(-\frac{0,557805}{28,4506}\right) = -1,55119$$

$$V_L(t) = 56,9121 \cdot e^{-1,84261 \cdot 10^4 t}$$

$$\text{no. } \omega_{\text{padding}}: T = \frac{-1,55 + j2,2 \cdot 10^{-4}}{5} = 2,13 \cdot 10^{-5} \text{ c. } 48,69 \cdot 10^4 \text{ Hz. - non-zero.}$$

$$V_L = E_2 - \frac{R_1 E_2}{R_1 + R_2} - \frac{R_2}{R_1 + R_2} J_L + \left(\frac{1}{R_1 + R_2} - 1 \right) V_C$$

$$\frac{dV_L}{dt} = \frac{dE_2}{dt} - \frac{R_1}{R_1 + R_2} \frac{dE_2}{dt} - \frac{R_2}{R_1 + R_2} \frac{di_L}{dt} + \left(\frac{1}{R_1 + R_2} - 1 \right) \frac{dV_C}{dt}$$

$$\frac{dV_L}{dt} = - \frac{R_2}{R_1 + R_2} \frac{di_L}{dt} + \frac{1}{R_1 + R_2} \frac{dV_C}{dt} - \frac{dV_C}{dt}$$

$$\frac{dV_L}{dt} = - \frac{R_2}{R_1 + R_2} \left(- \frac{R_1 R_2}{L(R_1 + R_2)} i_L - \frac{R_2}{L(R_1 + R_2)} V_C + \frac{R_2}{L(R_1 + R_2)} E_2 \right) + \left(\frac{1}{R_1 + R_2} - 1 \right) \left(\frac{R_2}{CR_3(R_1 + R_2)} i_L - \frac{R_1 + R_2 + R_3}{CR_3(R_1 + R_2)} V_C + \frac{1}{C(R_1 + R_2)} E_2 \right)$$

$$\frac{dV_L}{dt} = \frac{R_2}{R_1 + R_2} \cdot \frac{R_1 R_2 i_L - R_2 V_C + R_2 E_2}{L(R_1 + R_2)} + \left(\frac{1}{R_1 + R_2} - 1 \right) \left(\frac{R_2 R_3 i_L - (R_1 + R_2 + R_3) V_C + R_3 E_2}{CR_3(R_1 + R_2)} \right)$$

$$\frac{dV_L}{dt} = \frac{R_1 R_2^2 i_L - R_2^2 V_C + R_2^2 E_2}{L(R_1 + R_2)^2} + \frac{(1 - R_1 - R_2)(R_2 R_3 i_L - R_1 V_C - R_2 V_C - R_3 V_C + R_3 E_2)}{CR_3(R_1 + R_2)^2}$$

$$\frac{dV_L}{dt} = \frac{R_1 R_2^2 i_L - R_2^2 V_C + R_2^2 E_2}{L(R_1 + R_2)^2} + \frac{R_2 R_3 i_L - R_1 V_C - R_2 V_C - R_3 V_C + R_3 E_2 - R_2 R_3 i_L + R_1^2 V_C + R_1 R_2 V_C + R_3 R_1 V_C - R_3 R_2 E_2 + R_2^2 R_3 i_L}{L(R_1 + R_2)^2}$$

$$\frac{dV_L}{dt} = \frac{R_2}{R_1 + R_2} \left(\frac{R_1 R_2 E_2}{R_1 + R_3} - \frac{R_2 E_2 R_3 + R_2 E_2}{R_1 + R_3} \right) + \left(\frac{1}{R_1 + R_2} - 1 \right) \left(\frac{R_2 R_3 E_2}{R_1 + R_3} - \frac{(R_1 + R_2 + R_3) E_2 R_3 + R_3 E_2}{R_1 + R_3} \right)$$

B kombinirani c namennosti 5:

$$(0^+) \frac{dV_L}{dt} = -14025 \cdot 10^{-7} = -71283$$

$$(0^+) V_L = 569012$$

$$R_{EK} = \frac{E_2 R_2 - E_1 R_2}{2(R_1 + R_2)} = \frac{R_2 \Delta E}{2(R_1 + R_2)}$$

(VI)

$$J_k = \frac{E_1}{R_1 + R_3}$$

$$V_c = E_1 \cdot \frac{R_3}{R_1 + R_3}$$

$$V_k = E_2 - \frac{R_1 E_2}{R_1 + R_2} - \frac{R_2}{R_1 + R_2} J_k + \left(\frac{1}{R_1 + R_2} - 1 \right) V_c$$

$$\frac{dV_k}{dt} = - \frac{R_2}{R_1 + R_2} \frac{di_k}{dt} + \left(\frac{1}{R_1 + R_2} - 1 \right) \frac{dV_c}{dt}$$

$$\frac{dV_k}{dt} = + \frac{R_2}{R_1 + R_2} \left(\frac{R_1 R_2}{L(R_1 + R_2)} i_k + \frac{R_2}{L(R_1 + R_2)} V_c + \frac{R_2 E_2}{L(R_1 + R_2)} \right) + \left(\frac{1}{R_1 + R_2} - 1 \right) \left(\frac{R_2}{C(R_1 + R_2)} i_k - \frac{R_1 + R_2 + R_3}{C R_3 (R_1 + R_2)} V_c + \frac{E_2}{C(R_1 + R_2)} \right)$$

$$\frac{dV_k}{dt} = \frac{R_2}{R_1 + R_2} \left(\frac{R_1 R_2 i_k + R_2 V_c + R_2 E_2}{L(R_1 + R_2)} \right) + \left(\frac{1 - R_1 - R_2}{R_1 + R_2} \right) \left(\frac{R_2 R_2 i_k - (R_1 + R_2 + R_3) V_c + R_2 E_2}{C R_3 (R_1 + R_2)} \right)$$

$$\frac{dV_k}{dt} = \frac{R_1 R_2^2 i_k + R_2^2 V_c + R_2^2 E_2}{L(R_1 + R_2)^2} + \frac{(1 - R_1 - R_2) R_2 R_2 i_k - (1 - R_1 - R_2) (R_1 + R_2 + R_3) V_c + (1 - R_1 - R_2) R_2 E_2}{C R_3 (R_1 + R_2)^2}$$

$$\frac{dV_k}{dt} = \frac{C R_3 R_1 R_2^2 i_k + C R_3 R_2^2 V_c + C R_3 R_2^2 E_2 + (1 - R_1 - R_2) R_3 R_2 i_k - (1 - R_1 - R_2) (R_1 + R_2 + R_3) V_c + (1 - R_1 - R_2) R_2 E_2}{C R_3 L (R_1 + R_2)^2}$$

$$\frac{dV_k}{dt} = \frac{i_k (C R_3 R_1 R_2^2 + (1 - R_1 - R_2) R_3 R_2) + V_c (C R_3 R_2^2 - (1 - R_1 - R_2) (R_1 + R_2 + R_3) L) + E_2 (C R_3 R_2^2 + (1 - R_1 - R_2) R_2 L)}{C R_3 L (R_1 + R_2)^2}$$

$$\frac{dV_k}{dt} = (R_{EK} + j J_{EK}) (-\alpha + j\beta) e^{(-\alpha + j\beta)t} + (R_{EK} - j J_{EK}) (-\alpha - j\beta) e^{(-\alpha - j\beta)t}$$

$$t=0) = -2\alpha R_{EK} - 2\beta J_{EK}$$

$$\frac{dV_k}{dt} = -2\alpha R_{EK} - 2\beta J_{EK}$$

$$\frac{dV_k}{dt} = -2\alpha \frac{R_2 \Delta E}{2(R_1 + R_2)} - 2\beta J_{EK}$$

$$\frac{dV_k}{dt} = -\alpha \frac{R_2 \Delta E}{R_1 + R_2} - 2\beta J_{EK}$$

$$J_{EK} = -\frac{\alpha R_2 \Delta E}{R_1 + R_2} - \frac{dV_k}{dt}$$

$$V_k(t) = A_0 e^{-\alpha t} \cos(\beta t + \varphi_0)$$

$$A_0 = 2|K|$$

$$\varphi_0 = \arg K$$

$$T_c = 1,08 \cdot 10^{-5} = 11,62 \cdot 10^{-5} = \frac{10,59}{5} \cdot 10^{-5} = 2,108 \cdot 10^{-5}$$

$$f_c = 94743 \cdot 10^5 = 9,743 \cdot 10^4$$

$$\omega_0 = 2\pi f_c = 2,97260 \cdot 10^5 \text{ rad/s}$$

$$Q = \frac{\omega_0}{2\alpha} = \frac{2,97260}{2 \cdot 9,188679} = 7,933 \approx 8$$

$$2\alpha = \dots$$

(77)

$$1,9 \cdot 10^{-5} = 7,2 \cdot 10^{-5} \cdot 2\beta$$

$$\alpha = (7,2 - 1,9) \cdot 10^{-5} = 5,3 \cdot 10^{-5}$$

$$\alpha = 9,188679 \cdot 10^{-5} = 1,88679 \cdot 10^{-4}$$

- 1) anang ~~Dr.~~ Duman pp.
- 2) crabunus xapan ungrunnen polz. kocunpa.
- 3) upobeen anang plan yun. (crabun).

$$(0^-) i_L = -0,000946461$$

$$(0^-) v_C = -18,9671$$

$$(0^+) v_C = 56,9012$$

$$(0^+) \frac{dv_L}{dt} = -719836$$

$$\frac{di_L}{dt} = 20113,6$$

$$\frac{dv_C}{dt} = 699787$$

VII
Зачетное

$$ReK = 28,4506$$

$$ImK = -0,557005$$

$$2|K| = 56,9121$$

$$argK = -1,55119^\circ = -0,027073 \text{ рад}$$

$$\alpha = 1,21261 \cdot 10^4$$

$$\beta = 2,9458 \cdot 10^5$$

→ условие Ляпуна выполнено.

13